

CSE 31

Computer Organization

Lecture 25 – CPU Design (cont.)

Announcements


- Labs
 - Lab 10 grace period* ends this week
 - » Demo is **NOT REQUIRED** to receive full credit
- Reading assignments
 - **All** Reading (01-08) and Homework (01-06) assignments **open for submission till 09-MAY, 11:59pm**
 - » Complete **Participation/Challenge** Activities in each section to receive grade
 - » IMPORTANT: Make sure to submit score to CatCourses by using the link in the assignment page
 - » You may re-do past Reading/Homework assignments to improve score.

* A 10% penalty will be applied for late *submissions* during the grace period.

Announcements


- Project 02
 - Due 05-MAY
 - Can work in teams of 2 students
 - » Each team member must identify teammate in “Comments...” text-box at the submission page
 - » If working in teams, each student must submit code (can be the same as teammate) and demo individually
 - » Grade can vary among teammates depending on demo
 - Demo required for project grade
 - » No partial credit for submission without demo
 - **No grace period**
 - » **Must complete submission and demo by due date.**
- Extra Credit
 - Up to 2% towards your overall grades
 - **Due 06-MAY, 01:59am**
 - See assignment page on CatCourses for more details
- Lab with lowest score dropped from final grade evaluation

Generic Steps of Datapath (review)

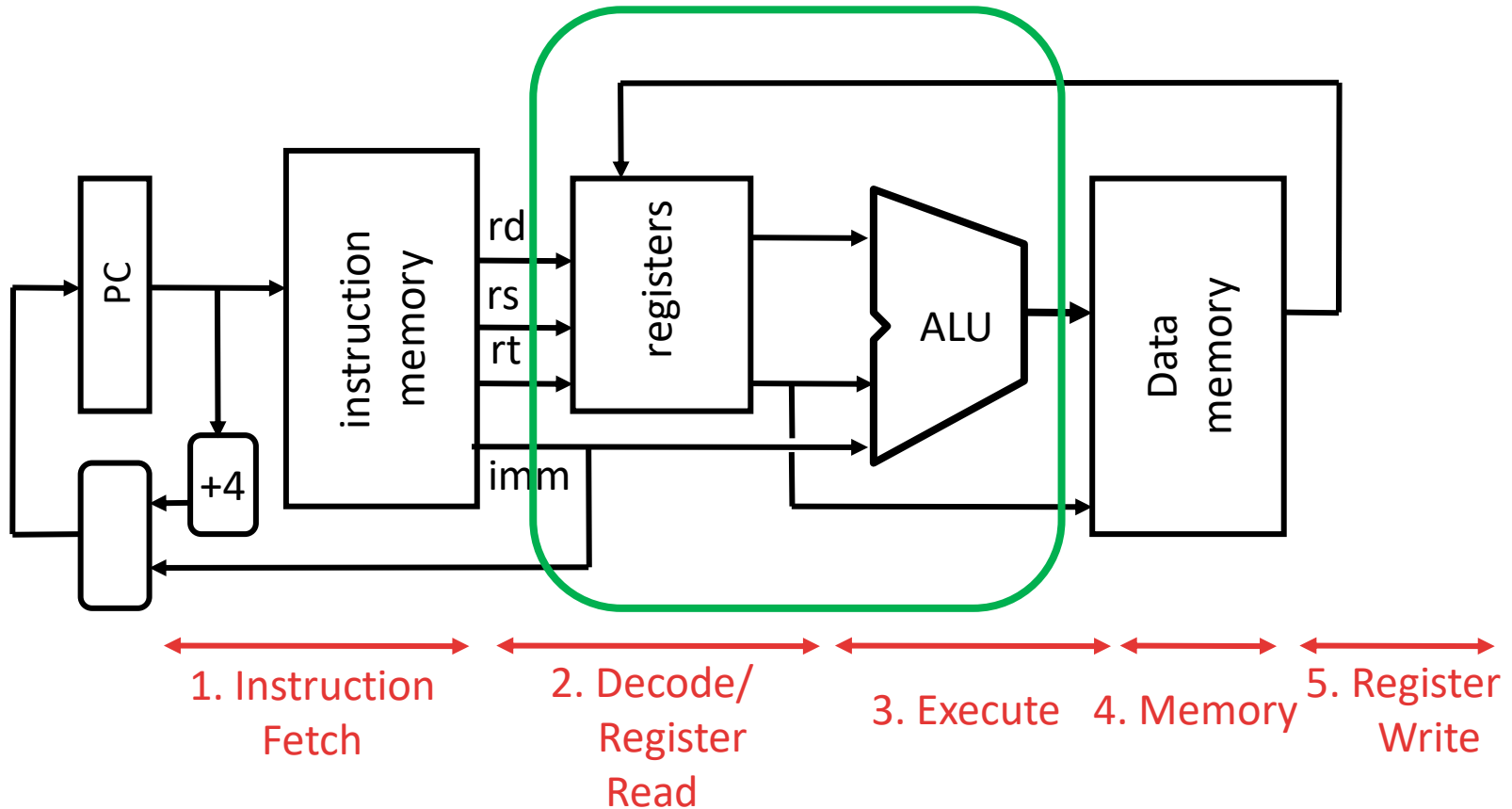


How do we handle the different register usage between r-type and i-type instructions?


Data Multiplexor or Mux (2-to-1, n-bits)

 

4-to-1 Multiplexor?

 


A zoomed in version of RegFile and ALU

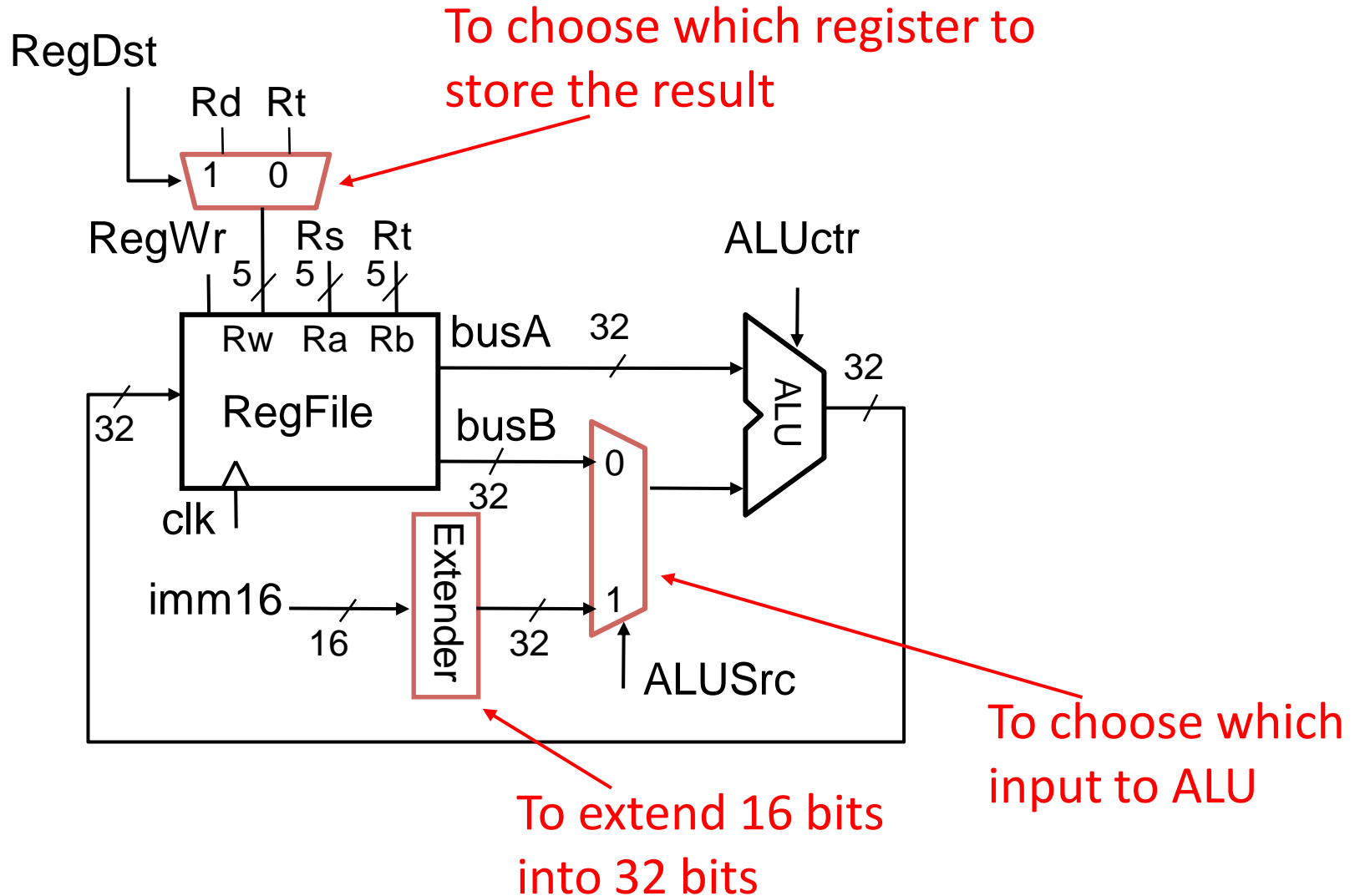


Operations with Immediate

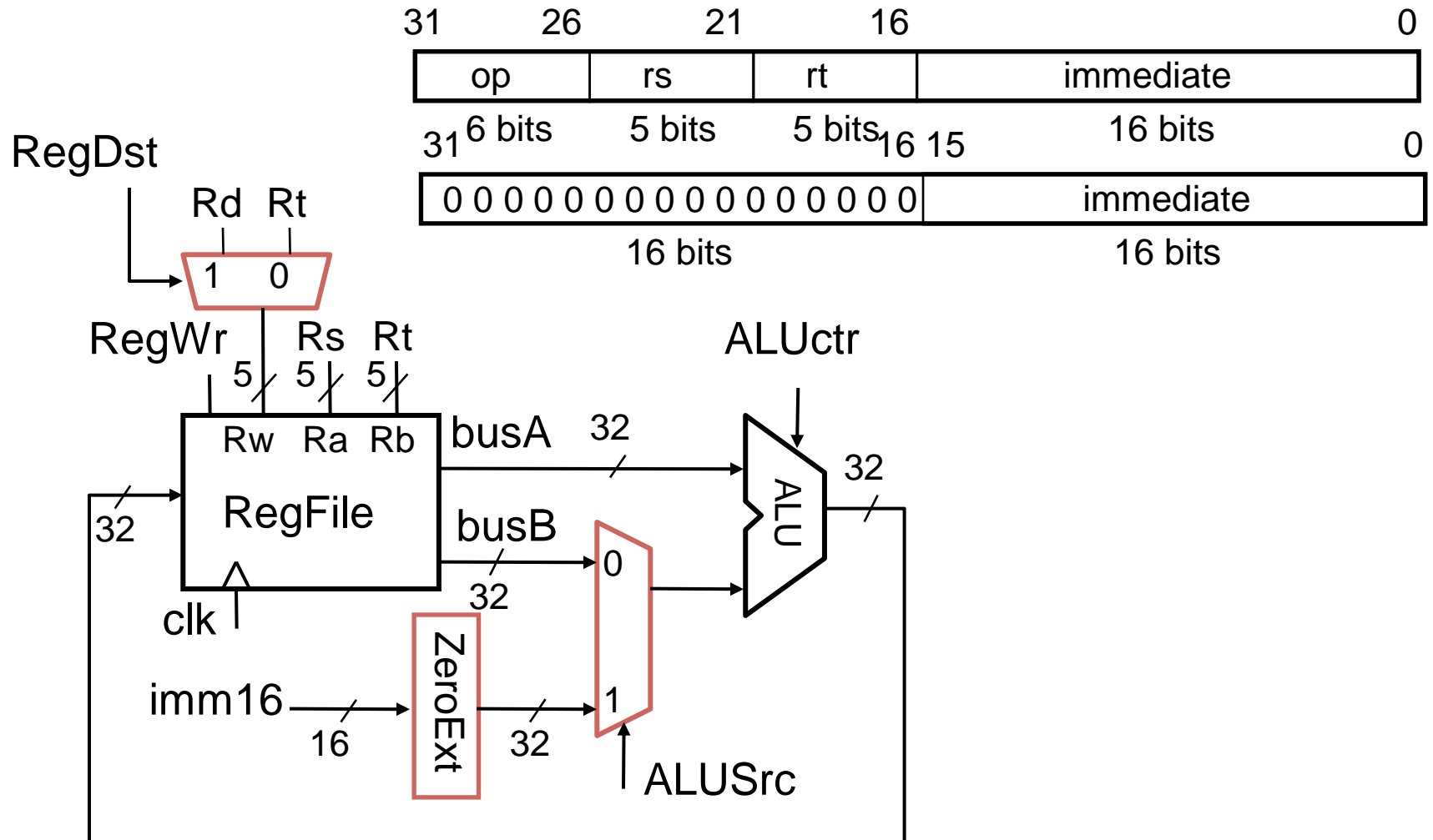- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



Operations with Immediate

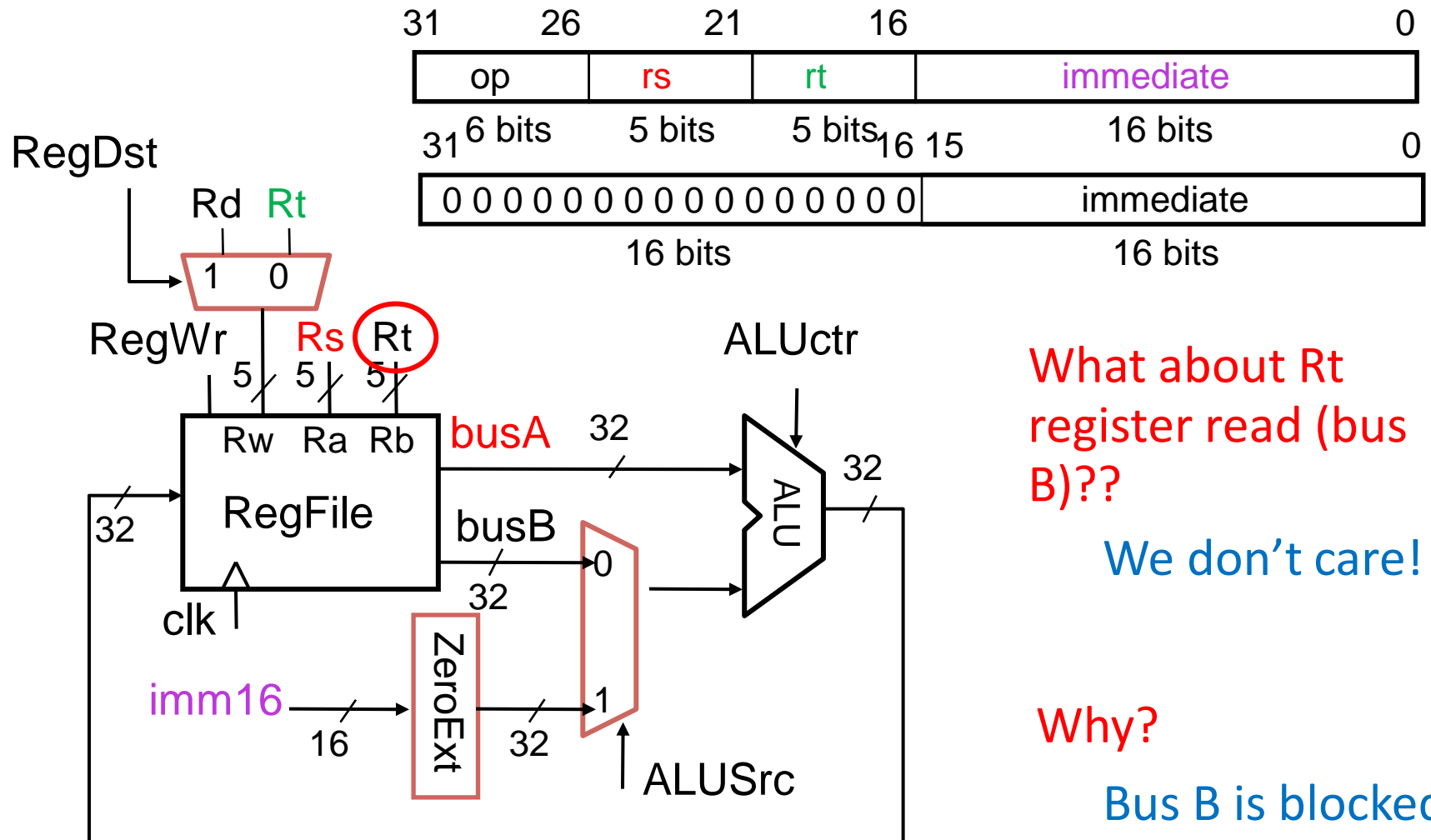- $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



What about Rt
register read (bus
B)??


We don't care!

Why?

Bus B is blocked

Load Memory

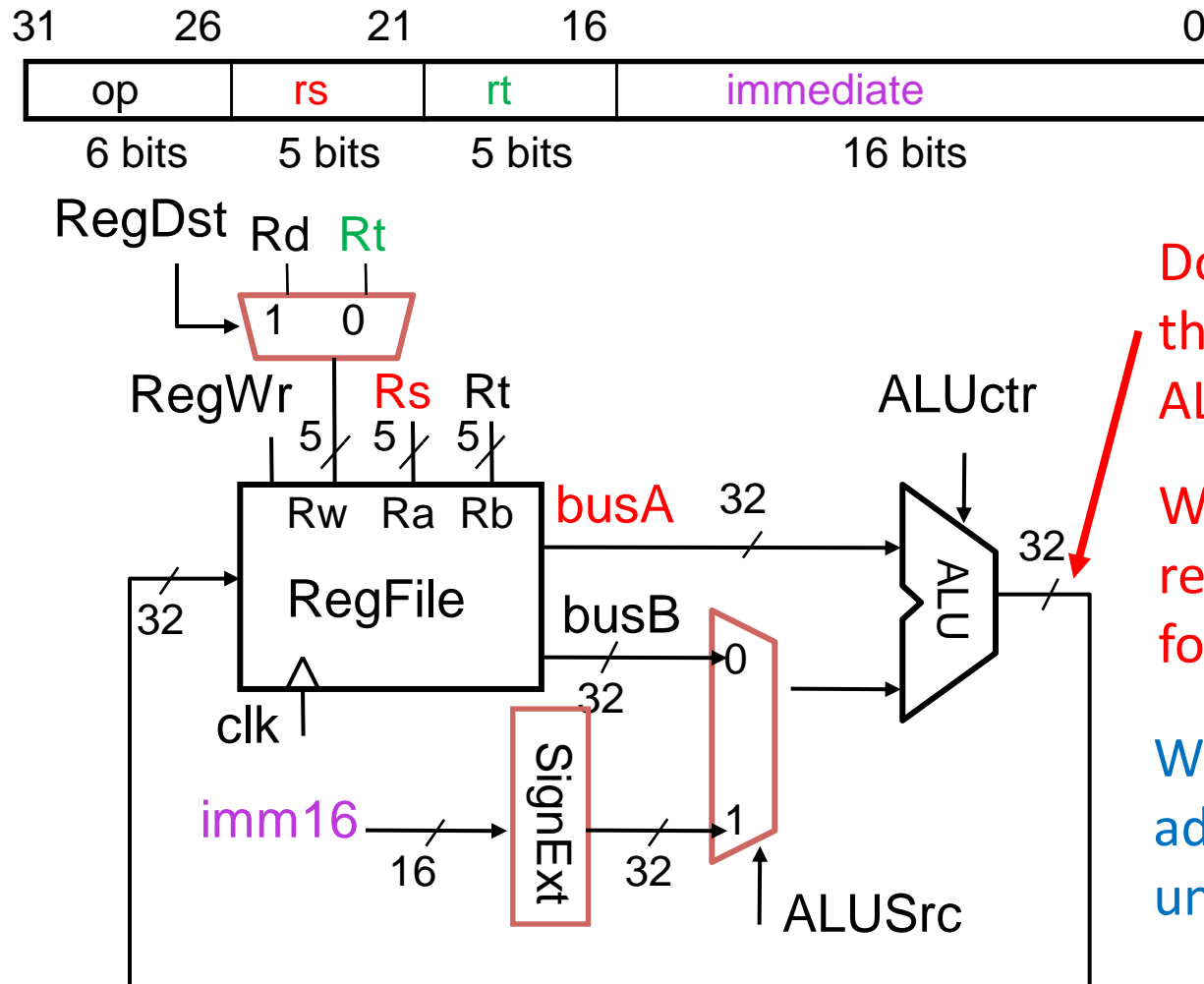- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
- Example: `lw rt, imm16(rs)`




Do we store
the result of
ALU?

What is the result of ALU for?

We need to
add a memory
unit!

Load Memory

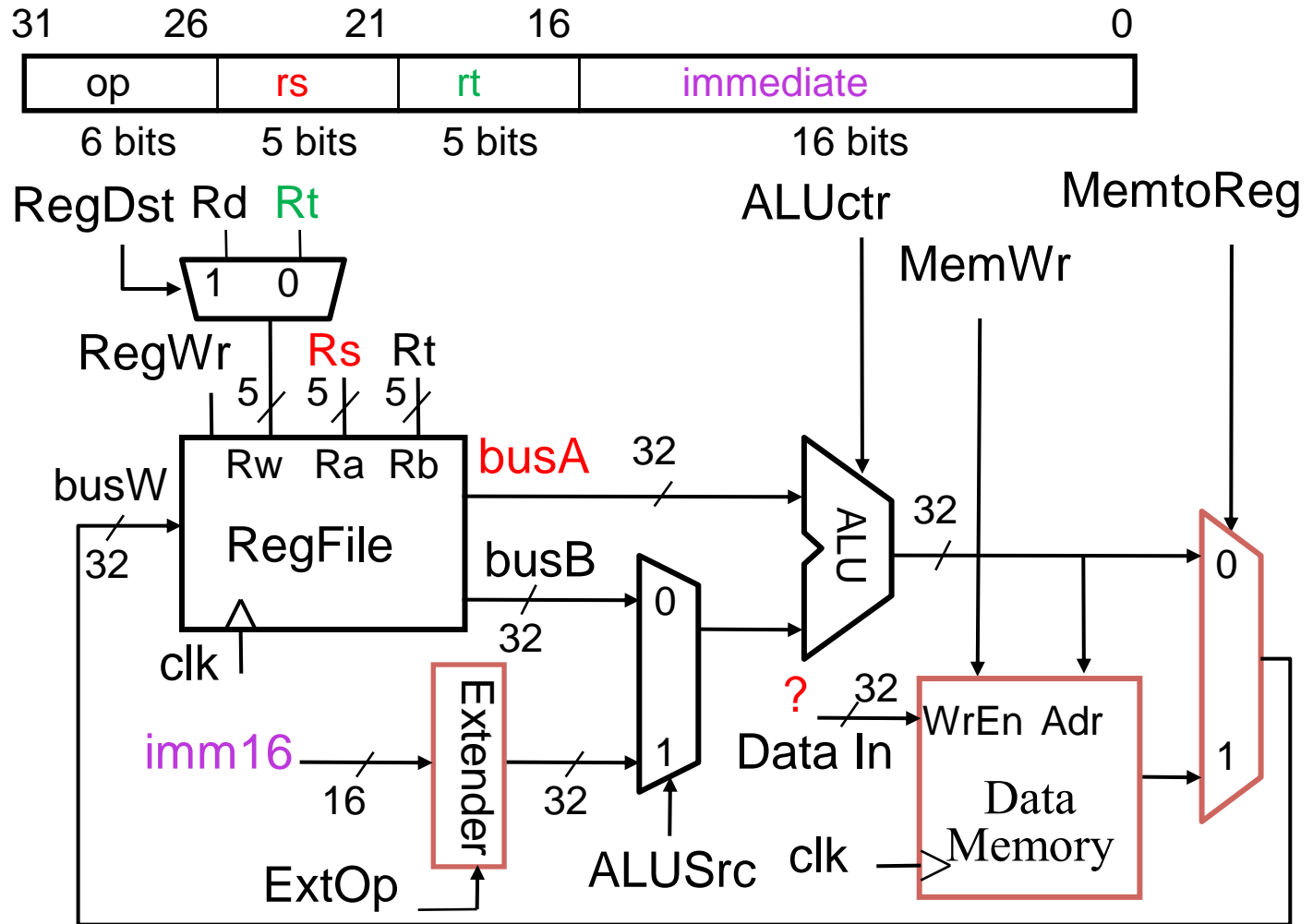
- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
- Example: `lw rt, imm16(rs)`



Store Memory

- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$



Ex.: `sw rt, imm16(rs)`

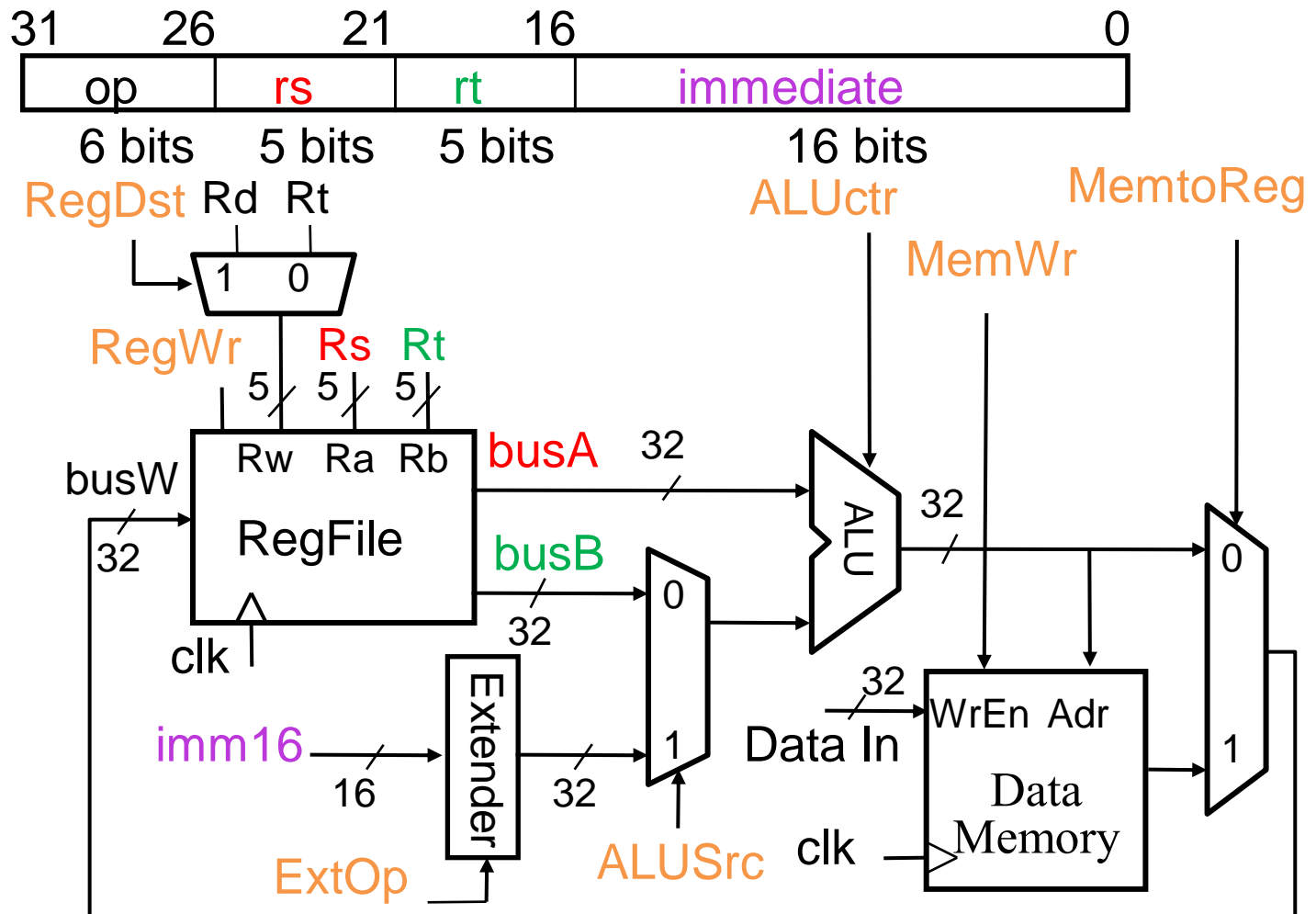

Store Memory

- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$



Ex.: `sw rt, imm16(rs)`

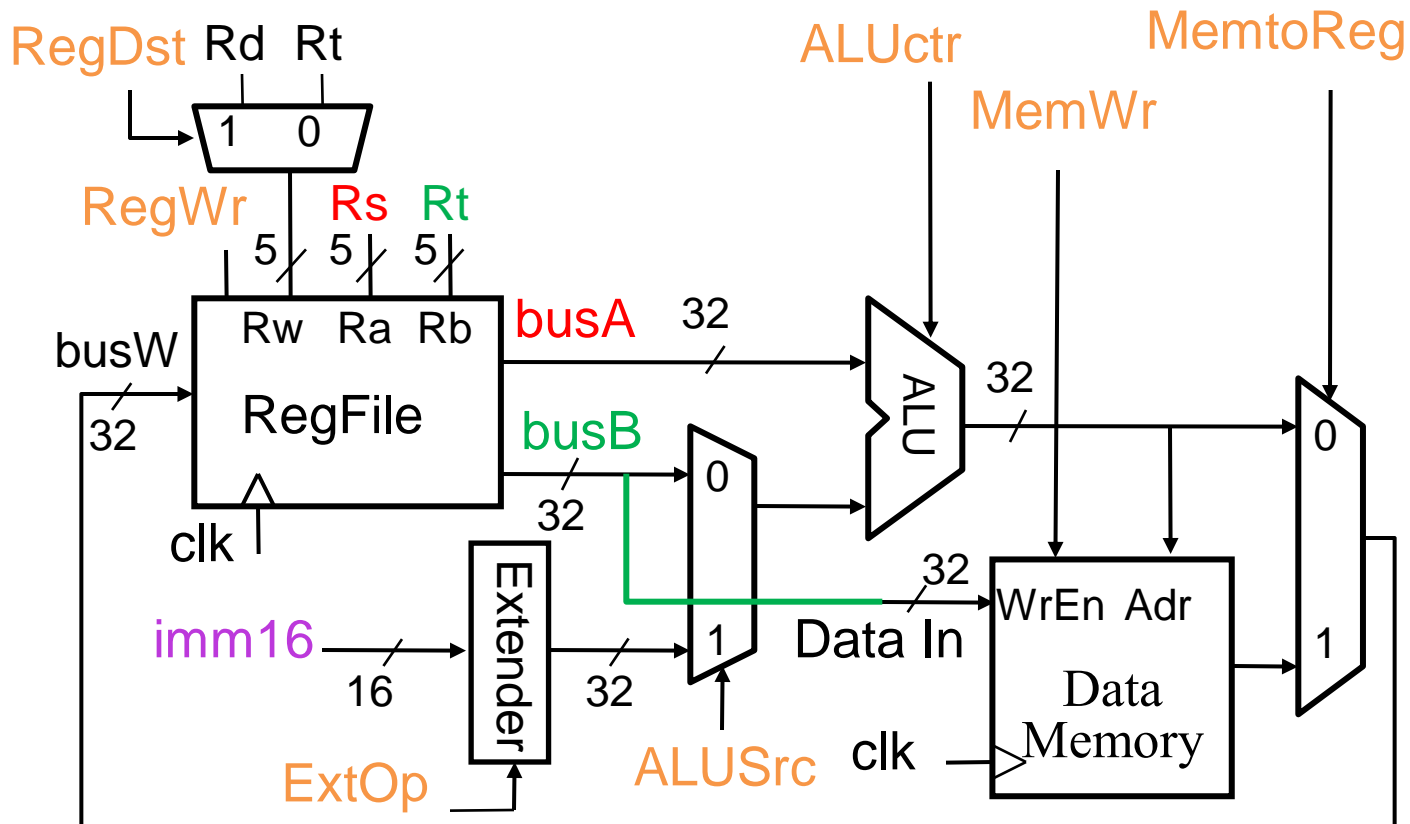 


Datapath for Branch Operations

- `beq rs, rt, imm16`


Datapath generates condition (equal)

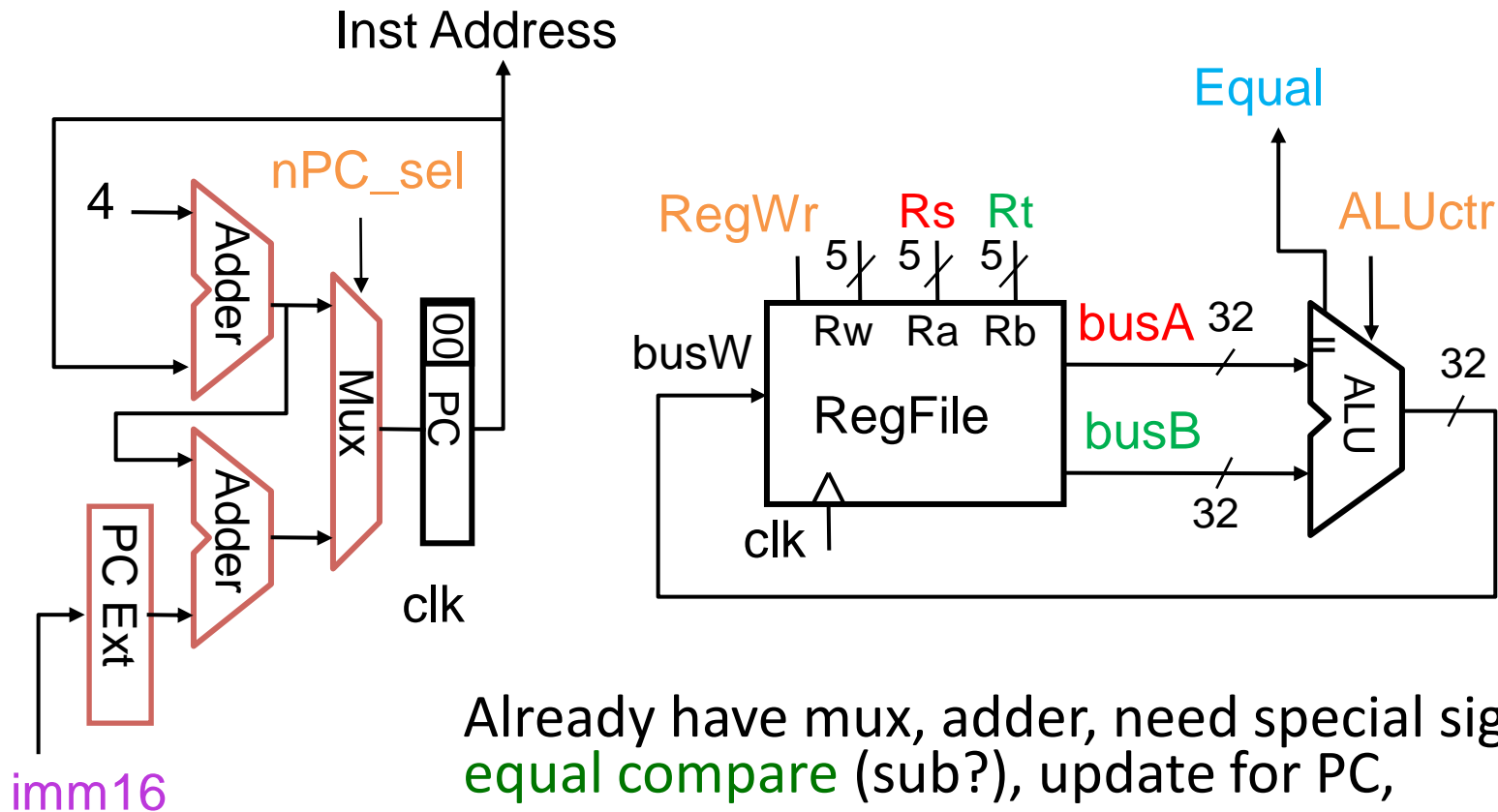 

Single Cycle Datapath

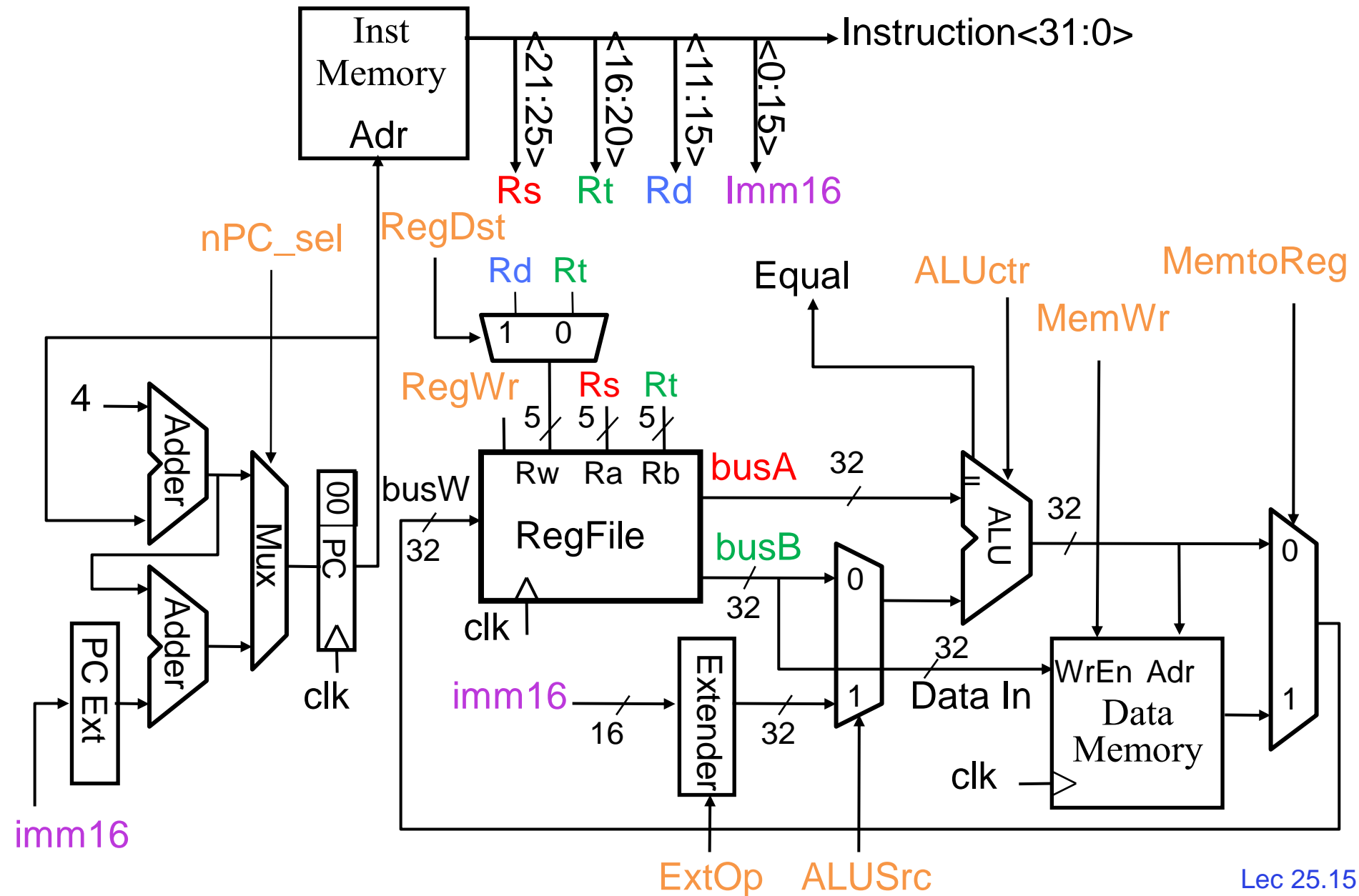


Abstract View of the Implementation

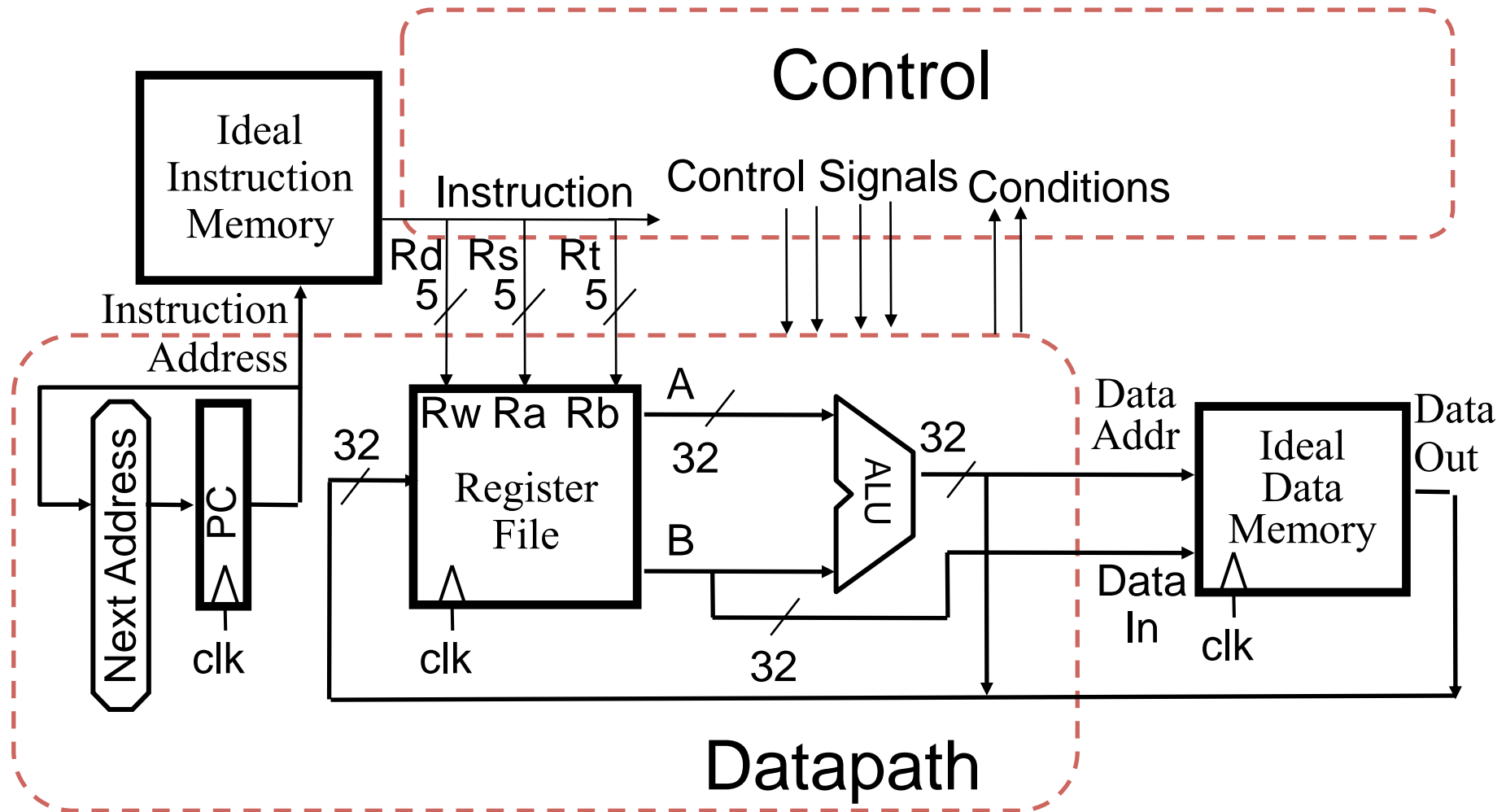


A Single Cycle Datapath

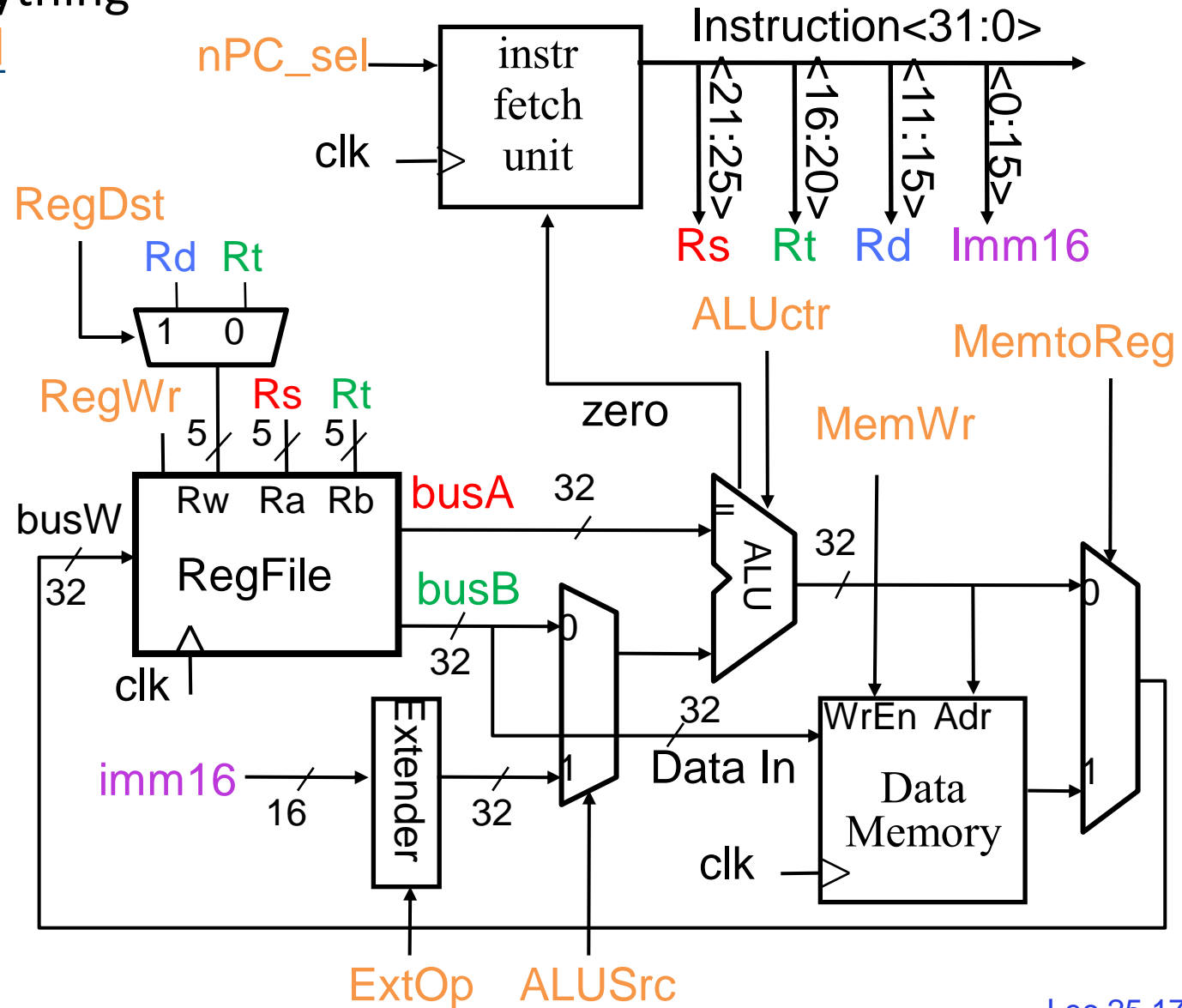- We have everything except control signals




Meaning of the Control Signals

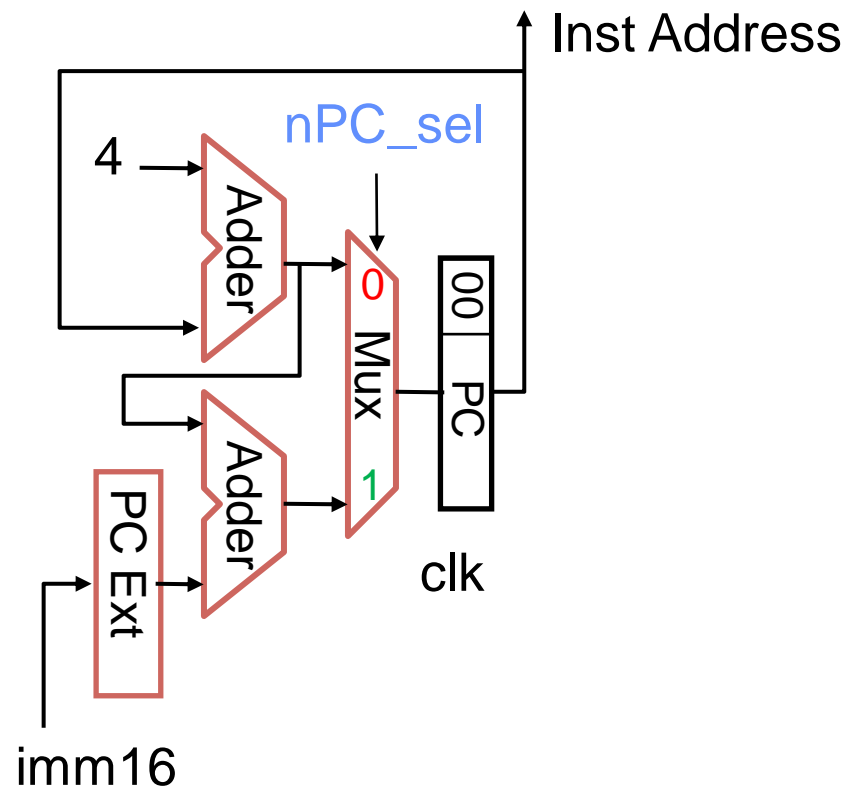- nPC_sel : “+4”: $0 \Rightarrow PC \leftarrow PC + 4$
“br”: $1 \Rightarrow PC \leftarrow PC + 4 + \{SignExt(Imm16), 00\}$
“n”=next
- Later in lecture: higher-level connection between mux and branch condition




Meaning of the Control Signals

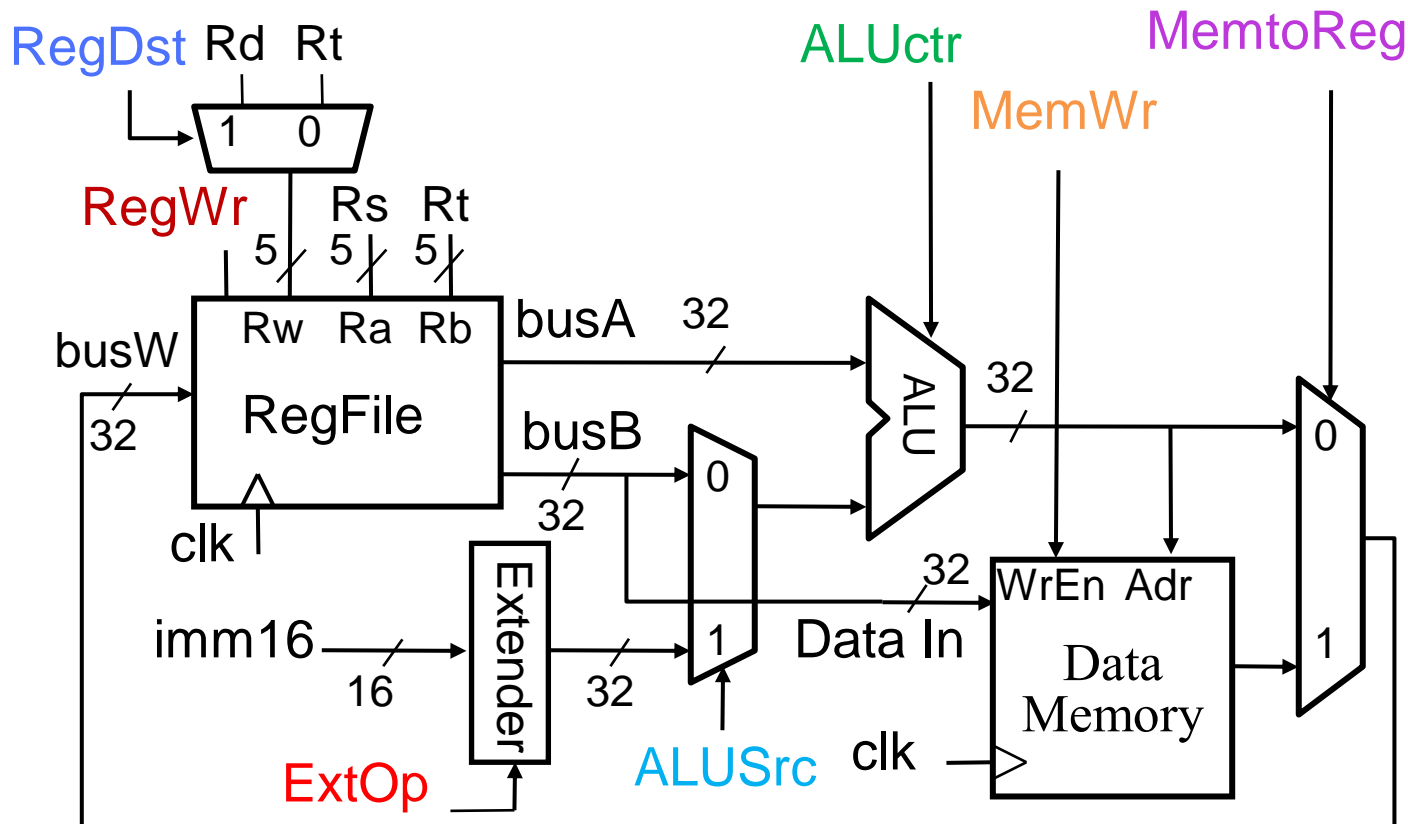- **ExtOp**: 0 \Rightarrow zero extend
1 \Rightarrow sign extend
- **ALUsrc**: 0 \Rightarrow regB;
1 \Rightarrow imm
- **ALUctr**: “ADD”, “SUB”, “OR”, ...
- **MemWr**: 1 \Rightarrow write memory
- **MemtoReg**: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst**: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr**: 1 \Rightarrow write register



The Add Instruction

 

add rd, rs, rt

– MEM[PC]

Fetch the instruction from memory

– $R[rd] = R[rs] + R[rt]$

The actual operation

– $PC = PC + 4$


Calculate the next instruction's address

Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


– same for all instructions

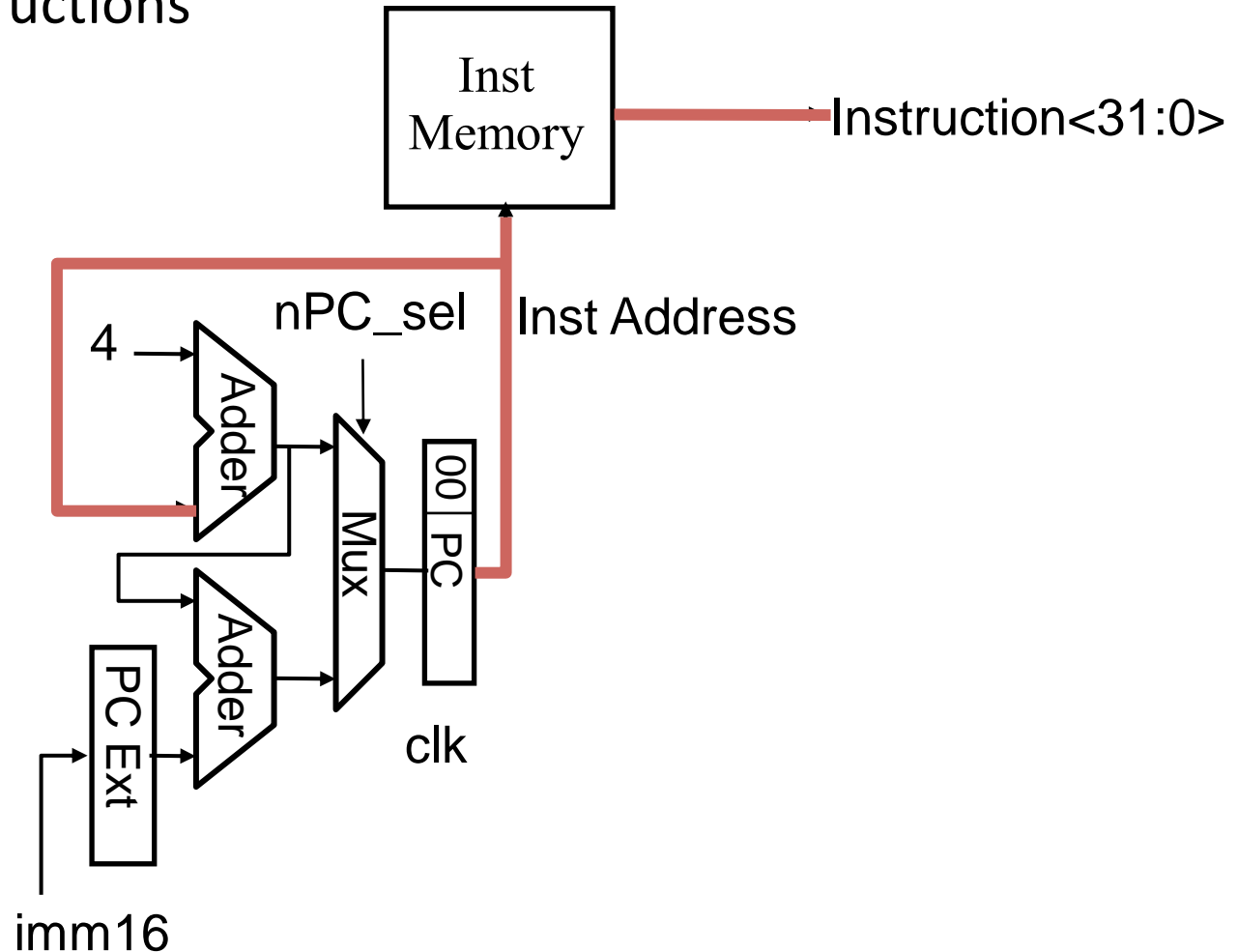

The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

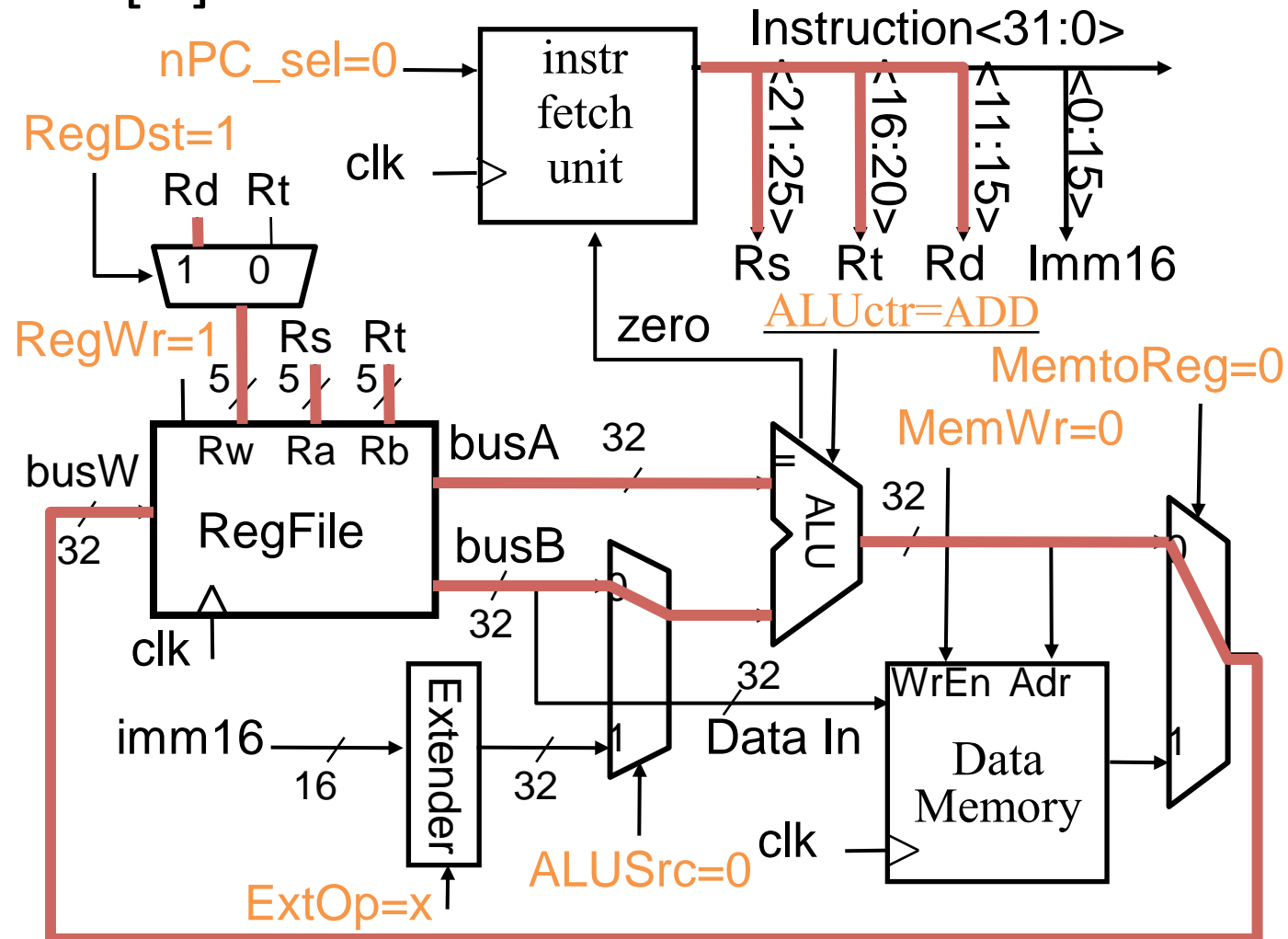


Instruction Fetch Unit end of Add

 
- $PC = PC + 4$
 - This is the same for all instructions except: Branch and Jump




Single Cycle Datapath for Ori

 

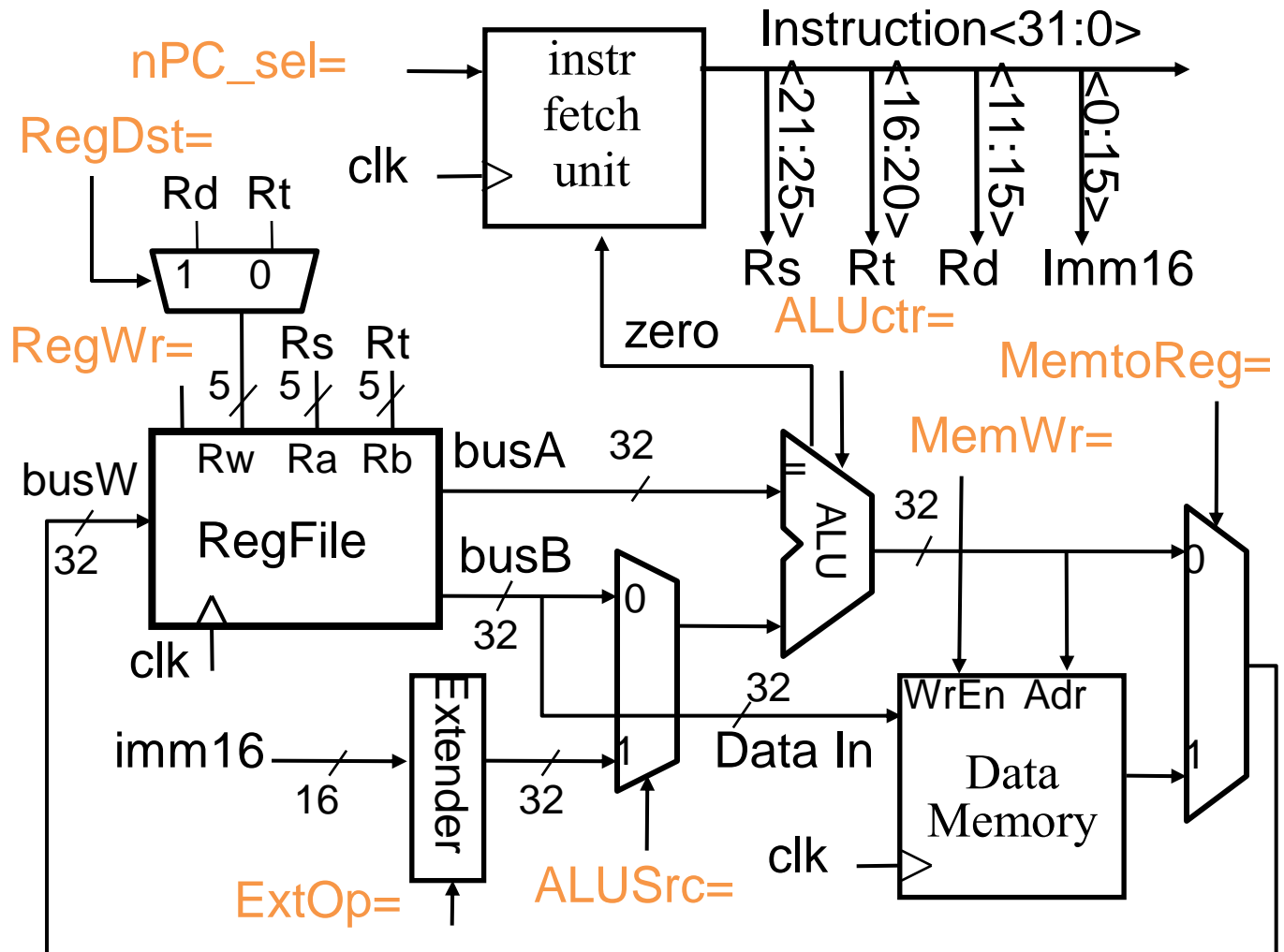
- $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for Ori

 

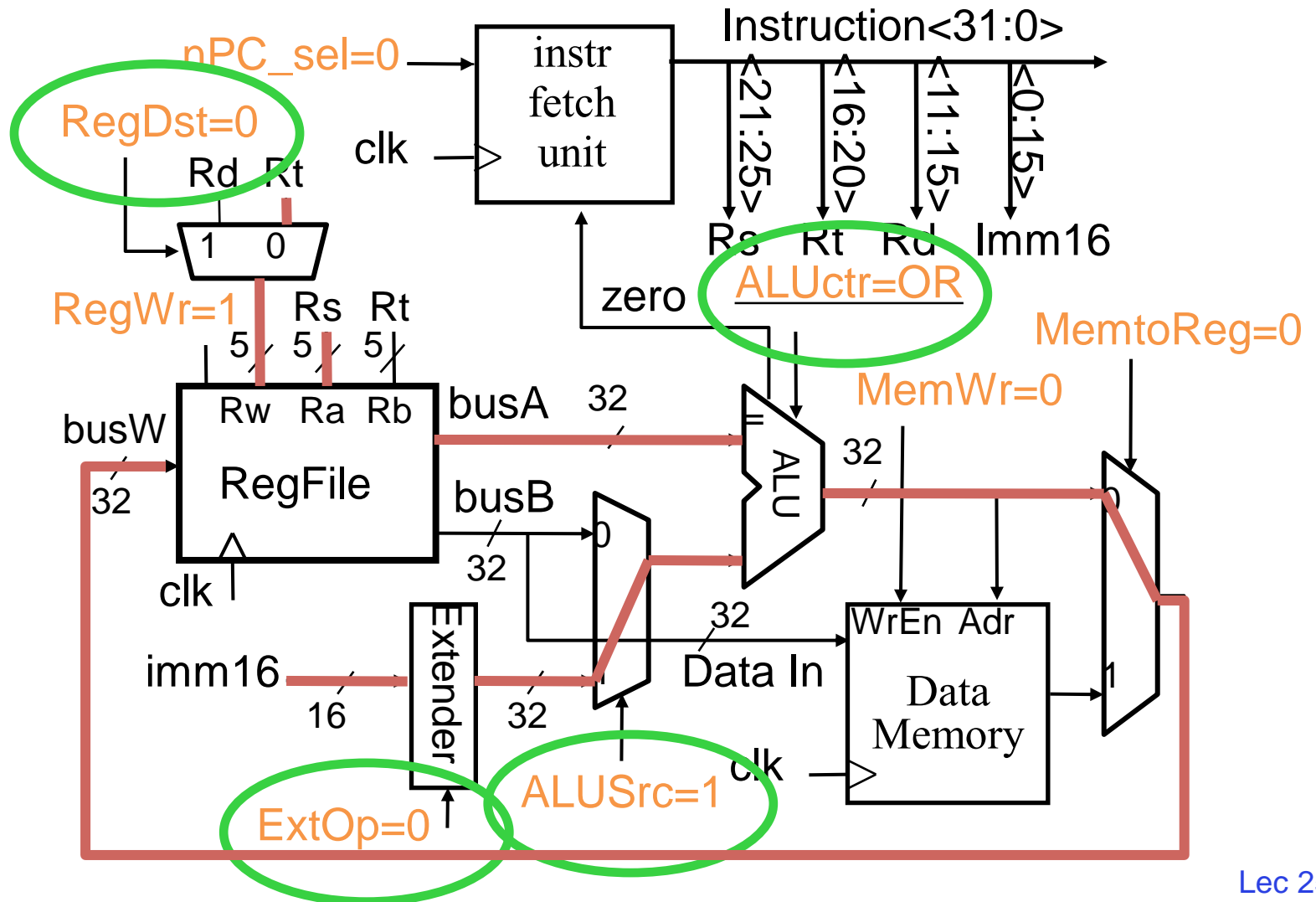
- $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for LW

 

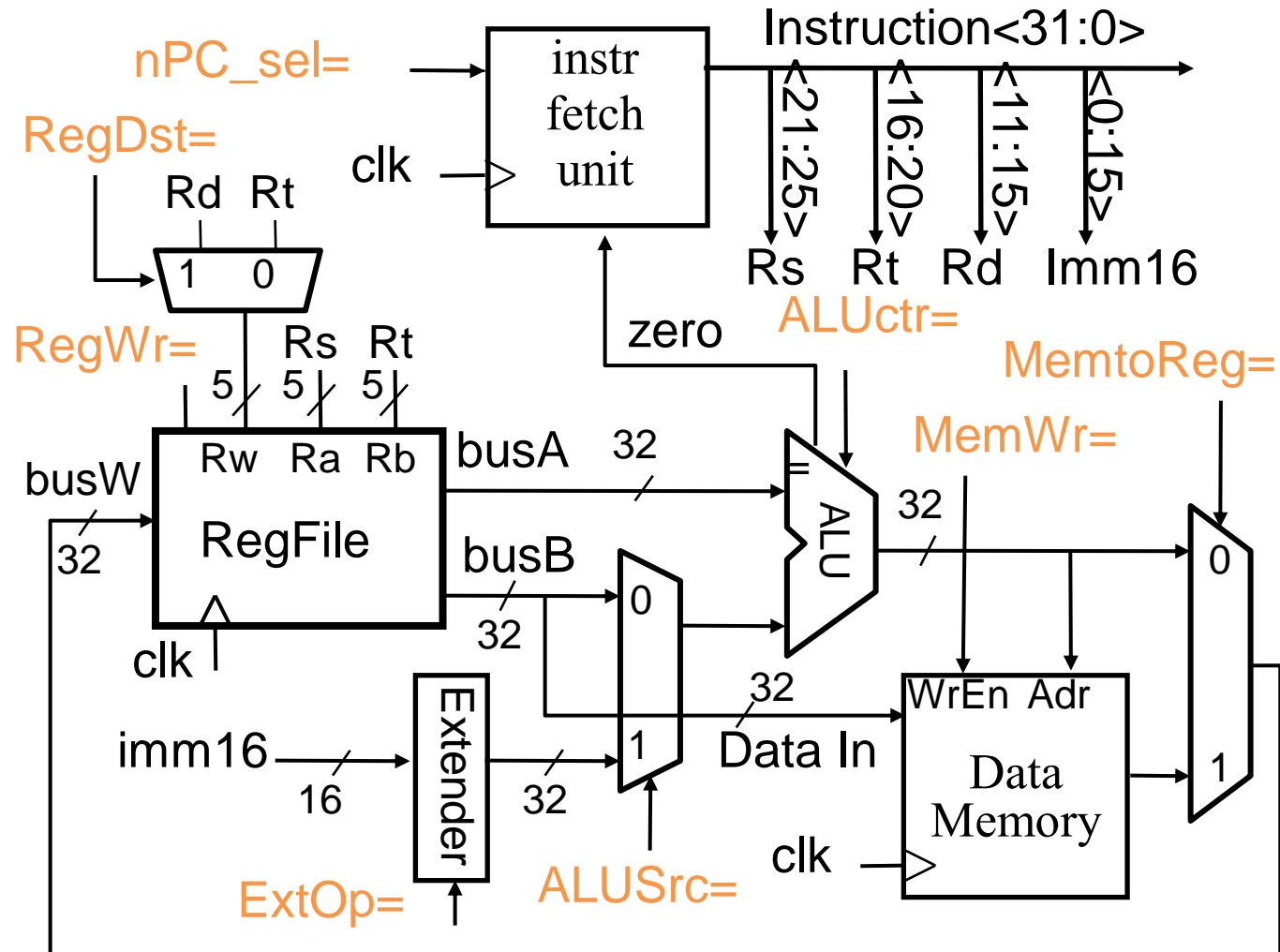
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for LW

 

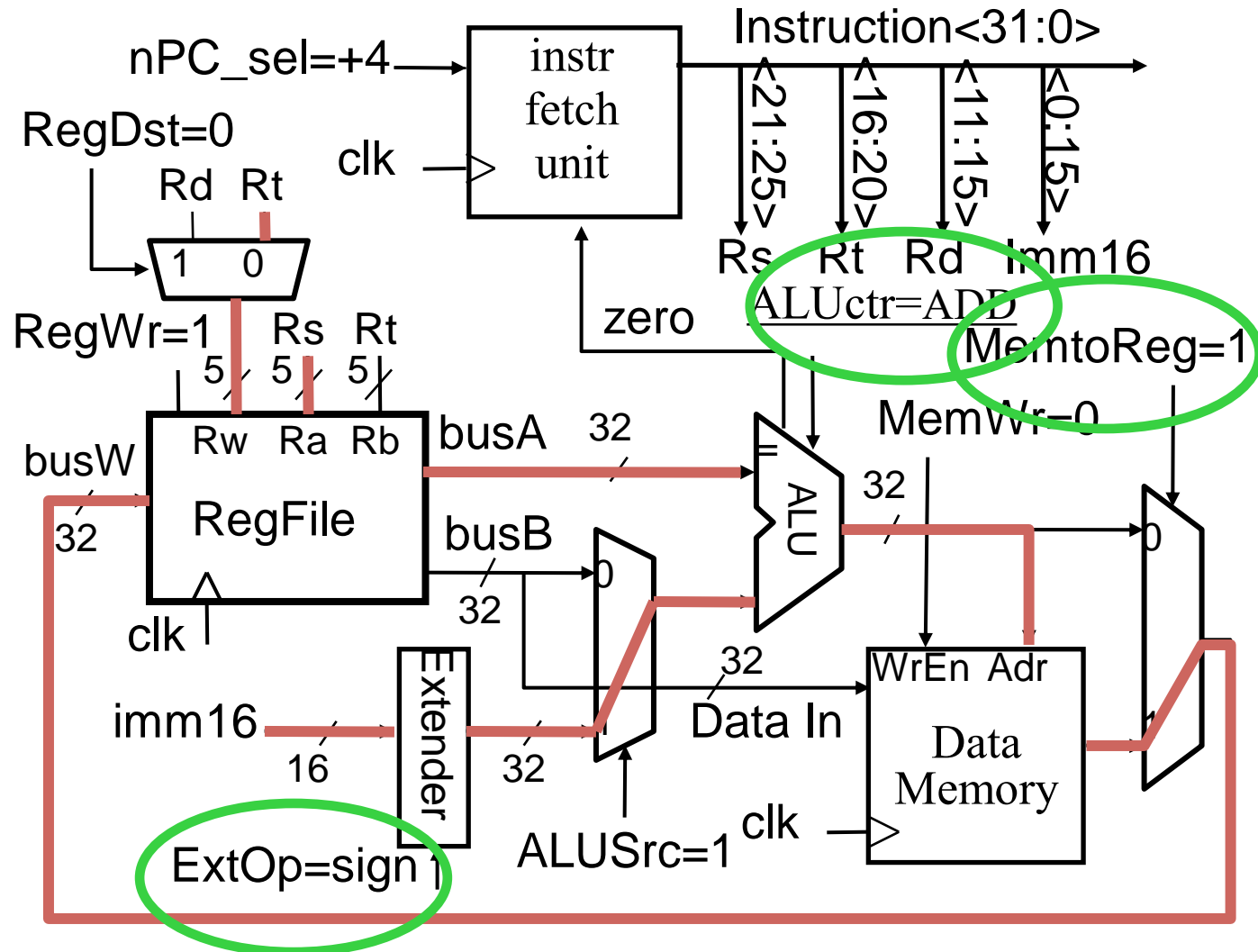
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for SW

 

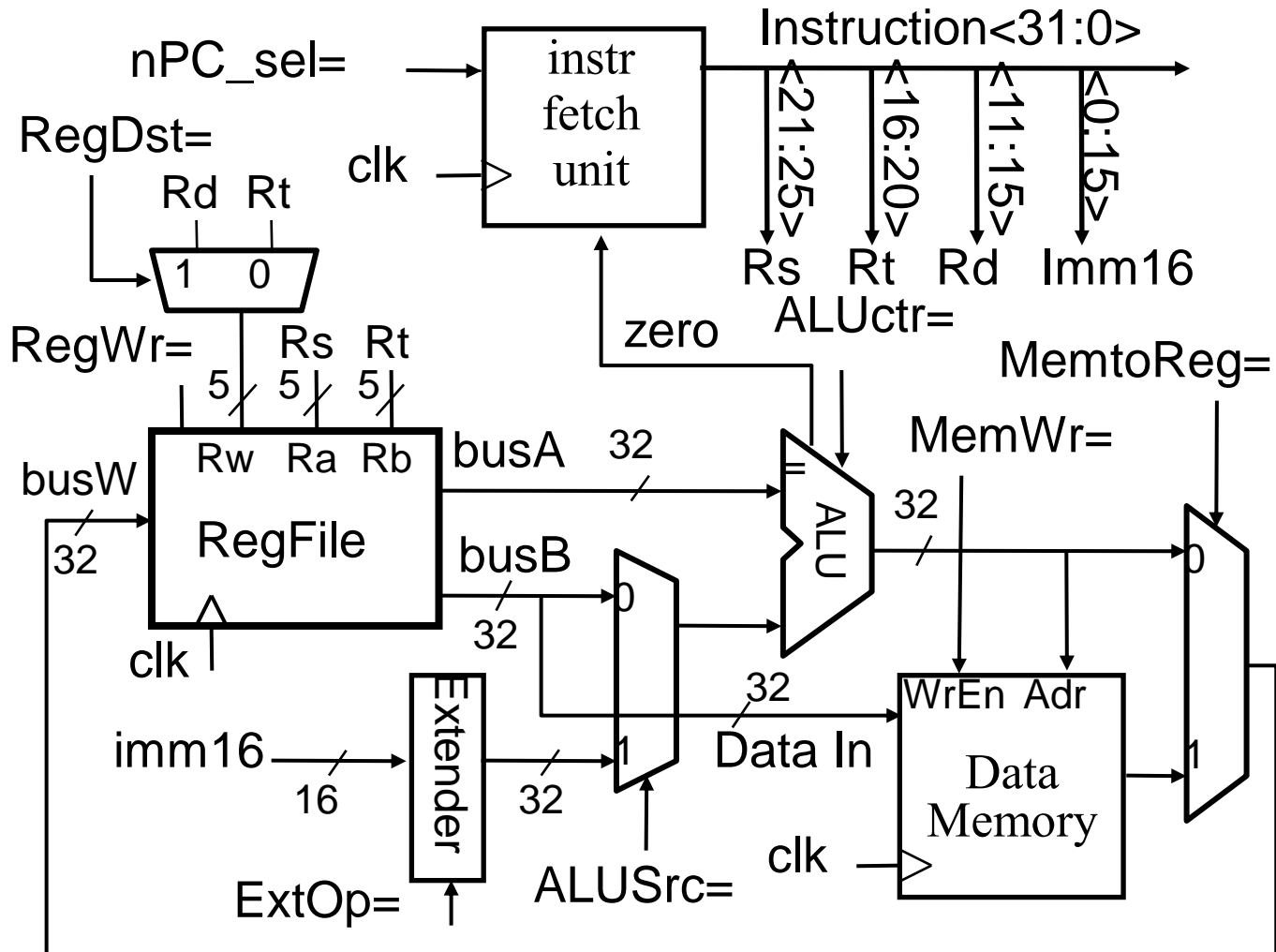- Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$



Single Cycle Datapath for SW

 

- Data Memory $\{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$

